

Mariam Sulakian
 CS 250 Homework #4
 Building a CPU
 29 March 2017

Test / File	Working
Arithmetic	Computed correct values with given tests for addi, add, sub.
Boolean	Computed addi, nand, xor functions correctly with given tests.
Control	<p>Performed addi, bgt, jal, beqz, and j functions correctly and passed given tests.</p> <p>The tests don't fully account for the jr instruction, but I believe my implementation should work; in my mux when I compute the address of the next PC, I set the jr instruction to compute the next PC address as the result of \$rs, specified by 's' from my regFile in the main circuit.</p>
io	Outputted correct results with given tests.
Memory	Performed lw, sw functions correctly. Passed given tests.
Shift	Both shl, shra performed as expected and passed given tests.
Register File (RegFile)	<p>Single 16-bit registers strung together correctly. Each register is constructed from 16 D-FlipFlops.</p> <p>Outputs are as expected into the RegFile from main.</p> <p>Register Decoder correctly selects Mux output.</p>
ALU	<p>16-bit Adder correctly displays output. Built from a 4-bit Adder which is built from 1-bit Adders.</p> <p>Subtractor works. Functions like adder but flips bits and adds 1.</p> <p>Left Shift displays shifted result correctly.</p> <p>Right Shift correctly shifts bits to the right by given amount.</p> <p>Mux functions in accordance to the opcode.</p>
Controller	Decodes opcodes correctly. Each output works as expected with the given instructions (i.e. jal output is 1 when the instruction opcode is 1101).
Sign Extender	Sign extends 6 bit input to 16 bits correctly.